




ANURAG GROUP OF INSTITUTIONS


(Formerly CVSR College of Engineering)
Venkatapur (V), Ghatkesar (M), Medchal (dist)
Department of Electrical and Electronics Engineering

B.Tech-Ist year
(Common to ECE,CSE,IT&AI)
BEE- Assignment questions

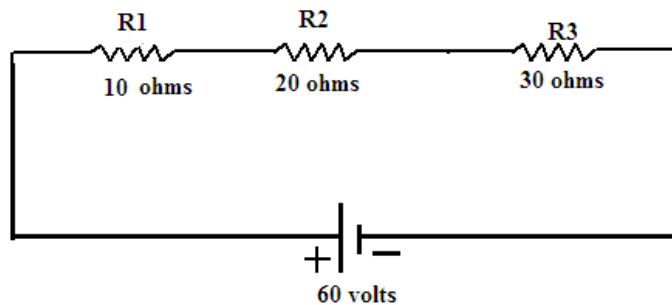
- 1) Derive the expressions for Star-Delta transformation and Delta-Star transformation?
- 2) a) Find the voltage across the three resistors shown in the figure



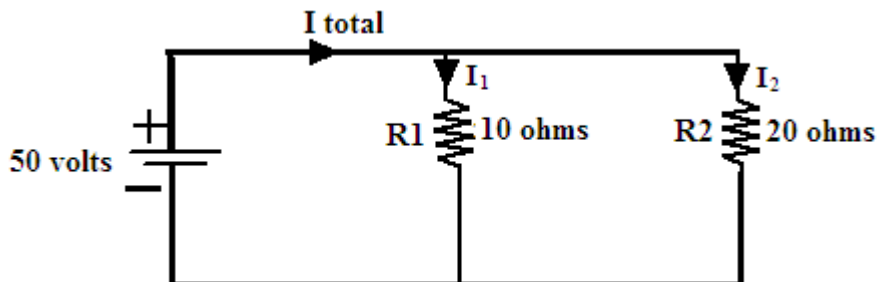
- b) Find the magnitude of total current, current through R1 and R2 if R1=10 ohms, R2=20 ohms and V= 50 volts as shown in the figure.



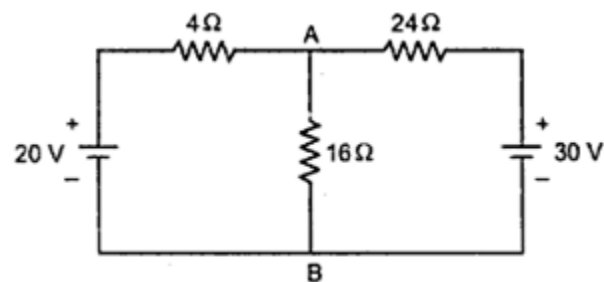
- 3) Using Super position Theorem, find the current passing through the 16 ohm Resistance?



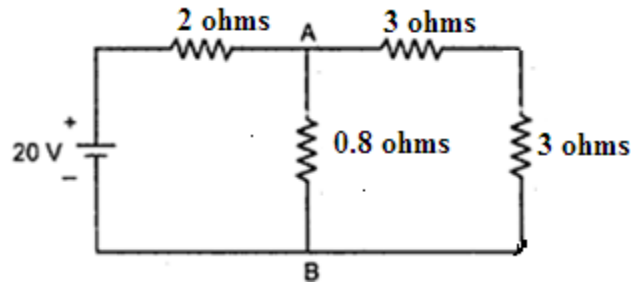
- 4) For the circuit shown in the figure, find the Thevenin's equivalent across 0.8 ohms resistance and hence find the current through it.



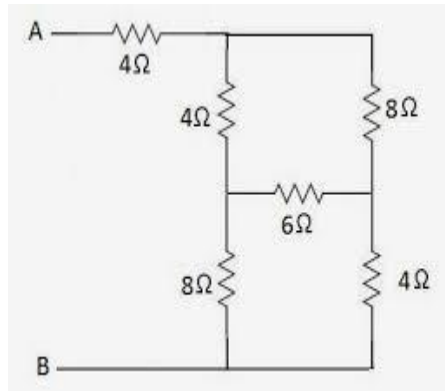- 5) a) Define i) Instantaneous Value ii) Peak Value iii) Frequency iv) Time Period.
 b) Derive Average and RMS values of Sine Wave & also Define form factor and peak factor.
- 6) Find Equivalent resistance between terminal A & B?



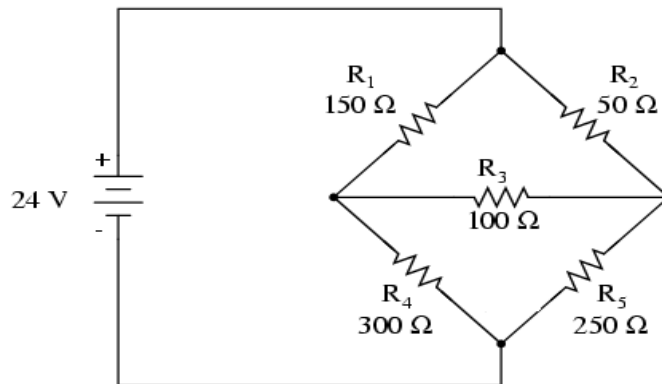- 7) State thevenin's theorem? By Using Thevenin's theorem, find the current in 100Ω resistor?



- 8) A series RL circuit with $R=100\ \Omega$, $L = 0.5\text{H}$ has an applied voltage of 230 V, 50Hz frequency. Calculate a) impedance b) current c) power factor d) Active power e) phasor diagram?

